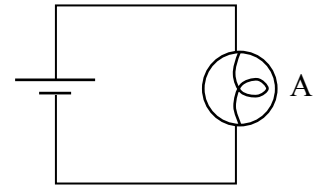


Resistor circuits

1. A bulb A is connected with ideal wires to an ideal battery as shown below.

a. Compare the potential difference across the bulb to the potential difference across the battery.

$$V_A = V_{\text{battery}}$$



b. Now two bulbs B and C, identical to the first one, are connected in series to the same battery. Compare:

- the current through bulbs B and C and through the battery.


$$I_B = I_C = I_{\text{battery}}$$

- the current through bulbs A (from section a), B and C.

$$I_B = I_C = \frac{I_A}{2}$$

- the potential difference across bulbs B and C and across the battery.
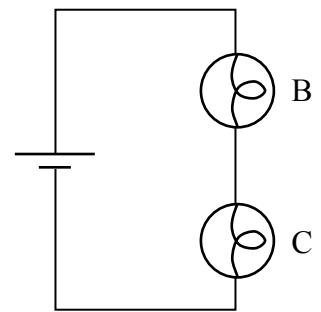
$$V_B = V_C = \frac{V_{\text{battery}}}{2}$$



- the potential difference across bulbs A, B and C.

$$V_B = V_C = \frac{V_A}{2}$$

- the brightness of bulbs A, B and C.


Brightness means power:

$$P_B = P_C = \frac{P_A}{4} \quad (P = I^2 R)$$

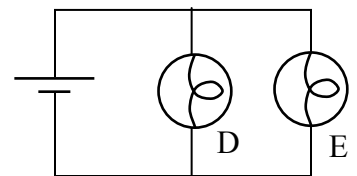c. Finally, two bulbs D and E, identical to the first one, are connected in parallel to the same battery. Compare:

- the current through bulbs D and E and through the battery.

$$I_D = I_E = \frac{I_{\text{battery}}}{2}$$



- the current through bulbs A (from section a), D and E.

$$I_D = I_E = I_A$$

- the potential difference across bulbs D and E and across the battery.

$$V_D = V_E = V_{\text{battery}}$$

- the potential difference across bulbs A, D and E.

$$V_D = V_E = V_A$$


- the brightness of bulbs A, D and E.

$$P_D = P_E = P_A$$

d. Does the current through an ideal battery depend on the circuit to which it is connected? *Yes.*

e. Does the potential difference across an ideal battery depend on the circuit to which it is connected? *No.*

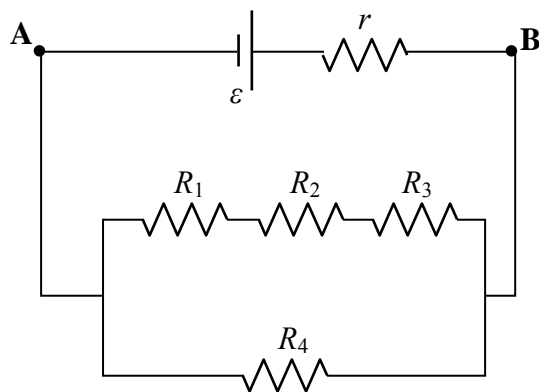2. An ideal battery of emf $\varepsilon = 12 \text{ V}$ is connected to five resistors r , R_1 , R_2 , R_3 and R_4 as shown in the figure below. The current through r is 0.45 A .



$$\begin{aligned} R_1 &= 10 \, \Omega \\ R_2 &= 20 \, \Omega \\ R_3 &= 30 \, \Omega \\ R_4 &= 40 \, \Omega \end{aligned}$$

Determine:

- The magnitude of r .

$$R_{1-2-3} = R_1 + R_2 + R_3 = 60 \Omega$$

$$R_{1-2-3-4} = \frac{1}{\frac{1}{R_{1-2-3}} + \frac{1}{R_4}} = 24 \Omega$$

$$R_{all} = R_{1-2-3-4} + r$$

$$i = \frac{\varepsilon}{R_{1-2-3-4} + r} \Rightarrow r = \frac{\varepsilon}{i} - R_{1-2-3-4} = \frac{12 \text{ V}}{0.45 \text{ A}} - 24 \Omega = 2.7 \Omega$$

b. The potential difference between points A and B.

$$V_A - V_B = iR_{1-2-3-4} = (0.45 \text{ A})(24 \Omega) = 10.8 \text{ V}$$

(or $V_A - V_B = \varepsilon - ir$)

c. The power produced by the battery.

$$P_{battery} = \varepsilon i = (12 \text{ V})(0.45 \text{ A}) = 5.4 \text{ W}$$

d. The power dissipated in resistor 2.

$$P = R_2 i_2^2$$

i_2 is the current through the top part of the parallel connection (ie, the current through R_1 , R_2 and R_3):

$$i_2 = \frac{V_A - V_B}{R_{1-2-3}} = \frac{10.8 \text{ V}}{60 \Omega} = 0.18 \text{ A}$$

Thus,

$$P = R_2 i_2^2 = (20 \Omega)(0.18 \text{ A})^2 = 0.65 \text{ W}$$